

F.3 Chapter 3 Solutions

3.1

	N-Type	P-Type
Gate=1	closed	open
Gate=0	open	closed

3.3 There can be 16 different two input logic functions.

3.5

A	B	C	OUT
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

3.7 There is short circuit (path from Power to Ground) when either $A = 1$ and $B = 0$ or $A = 0$ and $B = 1$.

3.9 The circuit is floating when $A = 0$ and creates a short-circuit when $A = 1$, which is guaranteed to burn out the power supply.

3.11 When $A = 0$, Out = 3.3 V

When $A = 1$, Out is floating, but power and ground are shorted, which will result in very high current and possible breakdown.

3.13 ***NOTE:** This problem was mistakenly included in Chapter 3 when it should belong in Chapter 5. See ERRATA for more information*


OUT = 1 signifies that the instruction is a branch instruction, and the branch will be taken. OUT = 0 means otherwise.

3.15


A	B	NOT(NOT(A) OR NOT(B))
0	0	0
0	1	0
1	0	0
1	1	1

AND gate has the same truth table.

3.17 a. Three input And-Gate

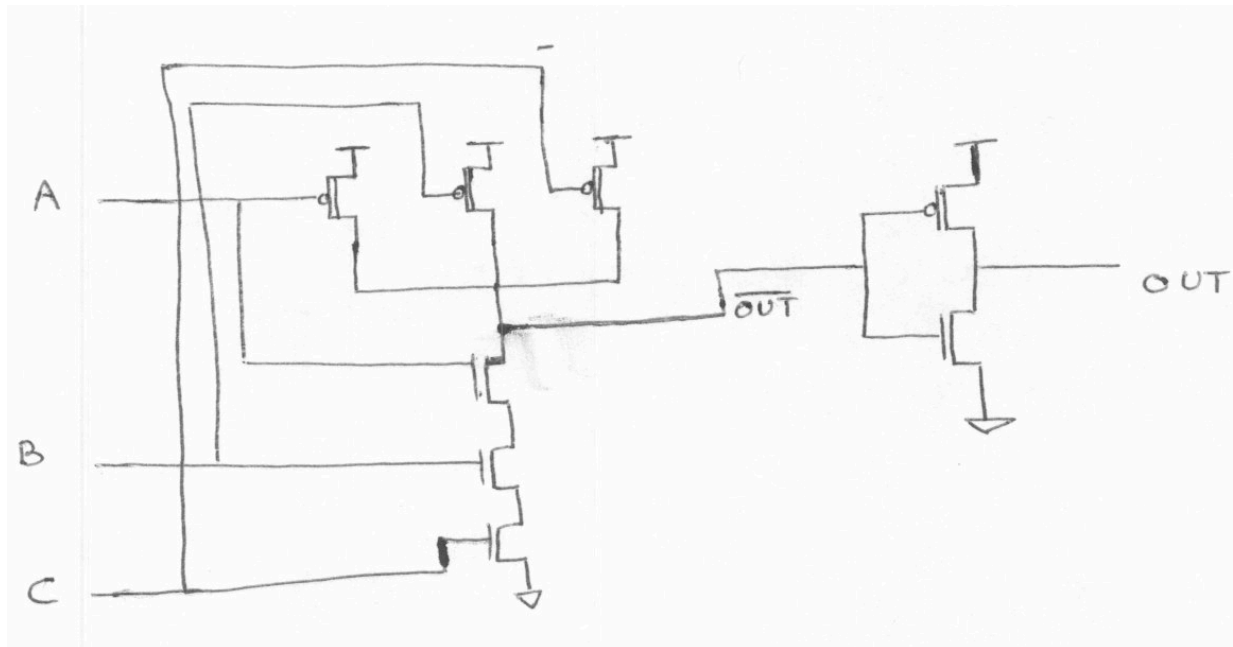


Three input OR-Gate

 


b. (1) $A = 1, B = 0, C = 0$.

AND Gate

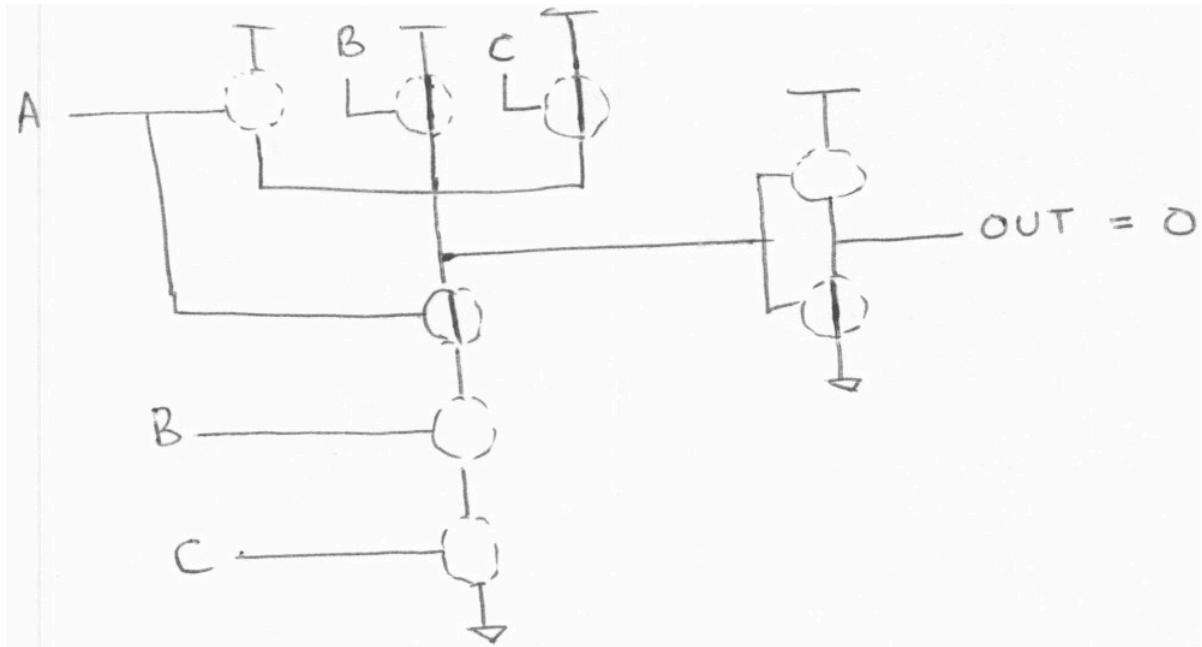


OR Gate

 


b. (2) $A = 0, B = 0, C = 0$

AND Gate

 


OR Gate

 


b. (3) $A = 1, B = 1, C = 1$

AND Gate

 

OR Gate

 

3.19 A five input decoder will have 32 output lines.

3.21

C _{in}	1	1	1	0
A	0	1	1	1
B	1	0	1	1
S	0	0	1	0
C _{out}	1	1	1	1

A = 7, B = 11, A + B = 18.


In the above calculation, the result (S) is 2 !! This is because 18 is too large a number to be represented in 4 bits. Hence there is an overflow - Cout[3] = 1.

3.23 (a) The truth table will have 16 rows. Here is the truth table for $Z = \text{XOR}(A, B, C, D)$. Any circuit with at least seven input combinations generating 1s at the output will work.

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$Z = \text{XOR}(A, B, C, D)$$

(b)

 

3.25 Figure 3.36 is a simple combinational circuit. The output value depends ONLY on the input values as they currently exist. Figure 3.37 is an R-S Latch. This is an example of a logic circuit that can store information. That is, if A, B are both 1, the value of D depends on which of the two (A or B) was 0 most recently.

3.27 $2 * 2^{14} = 2^{15} = 32768$ nibbles

3.29

A	B	C		Z
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		0
1	0	0		0
1	0	1		0
1	1	0		0
1	1	1		0

3.31 (a) 3 gate delays

3.31 (b) 3 gate delays

3.31 (c) $3 \times 4 = 12$ gate delays

3.31 (d) $3 \times 32 = 96$ gate delays

3.33(a) When $S=0$, $Z = A$

3.33(b) When $S=1$, Z retains its previous value.

3.33(c) Yes; the circuit is a storage element.

3.35 No. The original value cannot be recovered once a new value is written into a register.

3.37. $8 \times (2^3) = 64$ bytes

3.39.(a) To read the 4th memory location, $A[1,0] = 11$, $WE = 0$

3.39.(b) A total of 6 address lines are required for a memory with 60 locations. The addressability of the memory will remain unchanged.

3.39.(c) A program counter of width 6 can address $2^6 = 64$ locations. So without changing the width of the program counter, $64-60 = 4$ more locations can be added to the memory.

3.41 Total bits of storage $= 2^{22} \times 3 = 12582912$

3.43 There are a total of four possible states in this lock. Any other state can be expressed as one of states A, B, C or D. For example, the state performed one correct followed by one incorrect operation is nothing but state A as the incorrect operation reset the lock.

3.45 No. An arc is needed between the two states.

(a) Game in Progress:

Texas *	Oklahoma
Fouls:4	Fouls: 4
73	68
First Half	
7:38	
Shot Clock : 14	


(b) Texas Win:

Texas *	Oklahoma
Fouls:10	Fouls: 10
85	70
Second Half	
0:00	
Shot Clock : 0	

(c) Oklahoma Win:

Texas *	Oklahoma
Fouls:10	Fouls: 10
81	90
First Half	
7:38	
Shot Clock : 0	

3.47

 




3.49

a)

S1	S0	X		D1	D0	Z
0	0	0		0	0	0
0	0	1		0	0	0
0	1	0		0	0	1
0	1	1		1	0	1
1	0	0		1	1	1
1	0	1		1	1	1
1	1	0		1	0	1
1	1	1		1	0	1

b)

 

3.51 Flip-Flop


3.53

	0	1	2	3	4	5	6	7
Clock								
D2	0	1	1	1	1	0	0	0
D1	0	1	1	0	0	1	1	0
D0	0	1	0	1	0	1	0	1

The circuit is a decrementing 3-bit counter.

3.55

a	b	c	Y	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	1
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

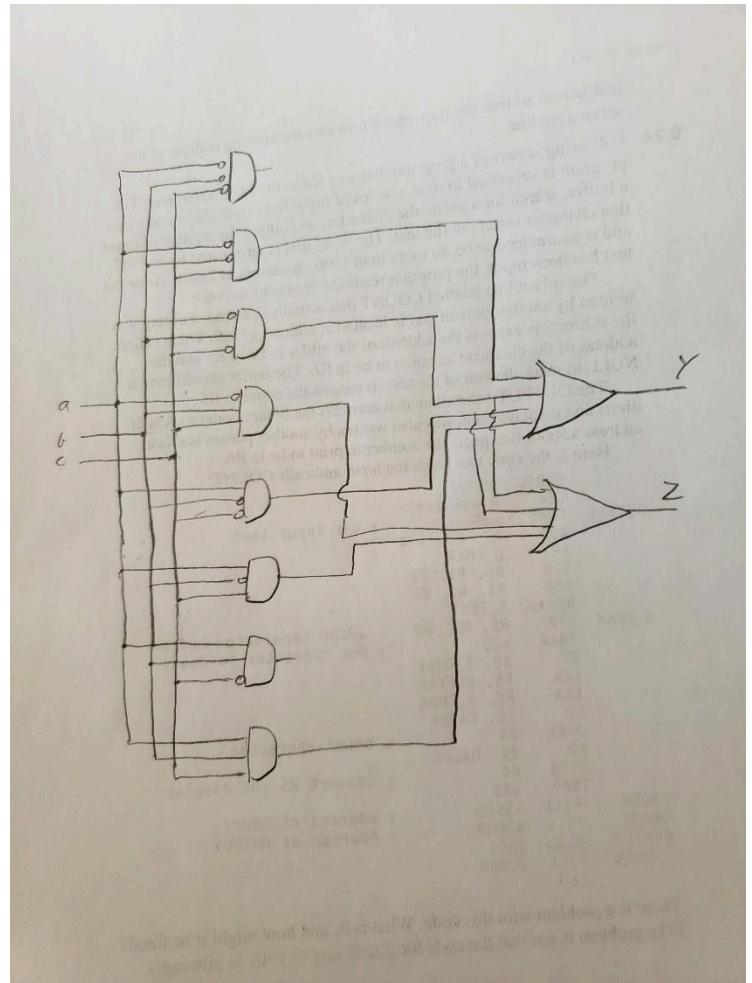


3.57


s[1]	s[0]	x	s'[1]	s'[0]	z
0	0	0	1	0	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	0

Copyri
written

d. No r

 

3.59

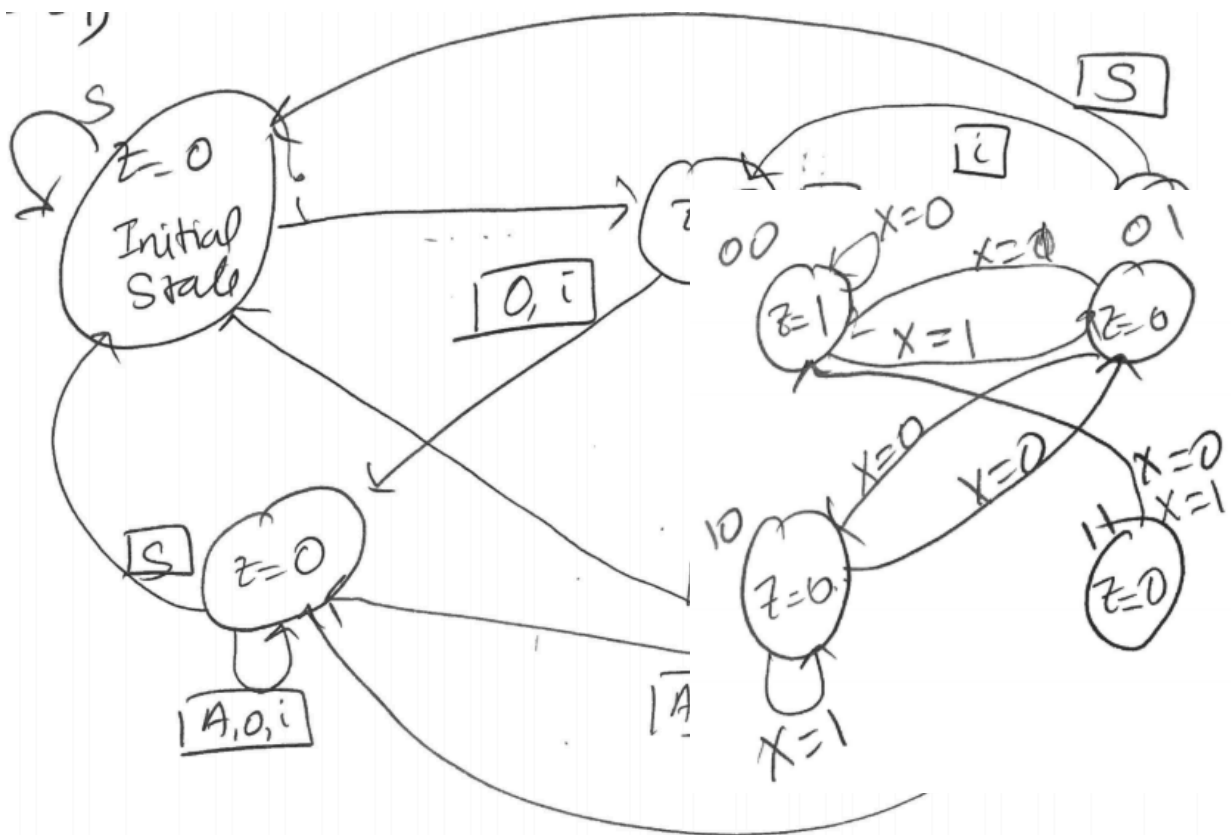

3.61